

Extra Credit

Due Date: August 23, 2019 by 5:00pm

MAT 022A Linear Algebra

Instructor: Mikhail Gaerlan


Instructions: This assignment is worth 15 extra points added to Midterm 1. The figure below is an electrical circuit diagram. Attached is the section on electrical circuits from *Introductory Linear Algebra: An Applied First Course*. Use Kirchoff's Circuit Laws to set up a system of equations for the currents $I_1, \dots, I_8$ in each wire. Then use Gaussian Elimination to solve the system. Make sure to write down each row operation used.

Nodes

- a. $I_4 = I_1 + I_7$
- b. $I_1 + I_2 = I_3$
- c. $I_5 = I_2 + I_4 + I_6$
- d. $I_3 + I_8 = I_5$
- e. $I_6 + I_7 = I_8$

Junctions

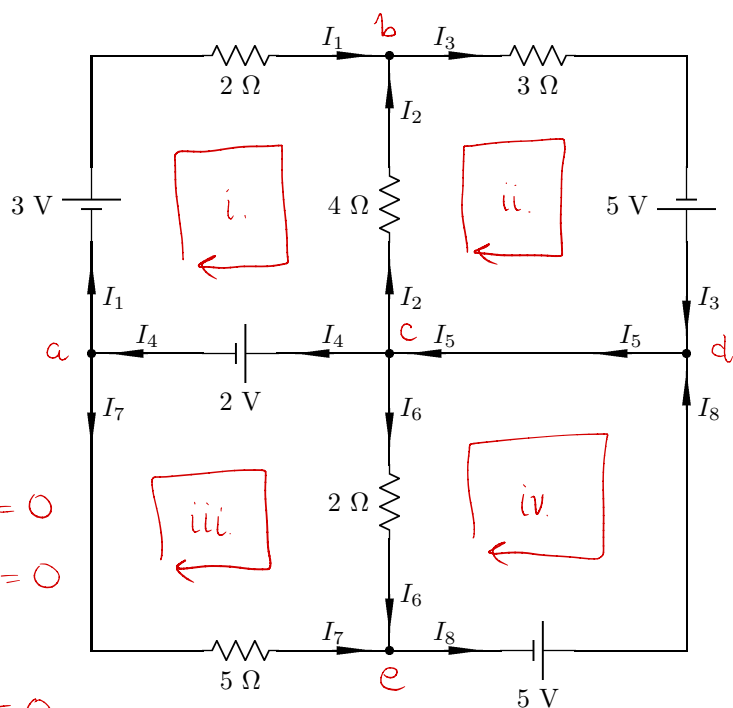- i. $3 - 2I_1 + 4I_2 - 2 = 0$
- ii. $-4I_2 - 3I_3 + 5 = 0$
- iii. $2I_6 - 5 = 0$
- iv. $2 - 2I_6 + 5I_7 = 0$



$$\begin{array}{c}
 I_1 \ I_2 \ I_3 \ I_4 \ I_5 \ I_6 \ I_7 \ I_8 \\
 \begin{array}{l}
 \text{a.} \\
 \text{b.} \\
 \text{c.} \\
 \text{d.} \\
 \text{e.} \\
 \text{i.} \\
 \text{ii.} \\
 \text{iii.} \\
 \text{iv.}
 \end{array}
 \begin{bmatrix}
 -1 & 0 & 0 & 1 & 0 & 0 & -1 & 0 \\
 1 & 1 & -1 & 0 & 0 & 0 & 0 & 0 \\
 0 & -1 & 0 & -1 & 1 & -1 & 0 & 0 \\
 0 & 0 & 1 & 0 & -1 & 0 & 0 & 1 \\
 0 & 0 & 0 & 0 & 0 & 1 & 1 & -1 \\
 -2 & 4 & 0 & 0 & 0 & 0 & 0 & 0 \\
 0 & -4 & -3 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & 2 & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & -2 & 5 & 0
 \end{bmatrix}
 \begin{array}{l}
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 -1 \\
 -5 \\
 5 \\
 -2
 \end{array}
 \end{array}$$

~

$$\begin{array}{c}
 I_1 \ I_2 \ I_3 \ I_4 \ I_5 \ I_6 \ I_7 \ I_8 \\
 \begin{bmatrix}
 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\
 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\
 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0
 \end{bmatrix}
 \begin{array}{l}
 \frac{27}{26} \\
 \frac{7}{26} \\
 \frac{17}{13} \\
 \frac{213}{130} \\
 \frac{573}{130} \\
 \frac{5}{2} \\
 \frac{3}{5} \\
 \frac{31}{10} \\
 0
 \end{array}
 \end{array}$$